

THAPAR UNIVERSITY, PATIALA
END-SEMESTER TEST

Subject: Power Quality & FACTS Devices (PS-005)

Session: Jan.-June, 2007

Course Instructor: Parag Nijhawan

M.Marks: 90

Time: 3hours

Instructions: *Attempt all questions.* The weightage of each question is indicated. Attempt all parts of one question at one place, otherwise, part(s) done at subsequent place(s) will be taken as over-attempt(s). Assume any missing data, if required. Notations have their usual meaning.

NOTICE: Evaluated answer sheets will be shown to the students on 29/05/2007 at 10.30AM in C-104.

- 1) a) What is 'electric power quality'? What are the various causes of power quality problems? Discuss in detail.
b) Obtain the PIM model for Static Synchronous Series Compensator. (9,9)
- 2) a) What are the major concerns of both power customers and utility? Discuss these in detail.
b) What is a CBEMA curve? What is the purpose of this curve? (12,6)
- 3) a) Prove that active power is a function of voltage phase angle and reactive power is a function of voltage magnitude.
b) Draw the block diagram of a UPFC and also discuss the purpose of two converters of the UPFC.
c) What is the principle of operation of a phase shifter? Also, draw the characteristic curves of the phase shifter. (6,6,6)
- 4) a) Discuss how converter fed d.c. drives act as source of harmonics.
b) Discuss the complete analysis of single-phase active filter, including the control circuit of the DC bus-bar voltage. (6,12)
- 5) Write short notes on the following:
 - a) Modulated Phase Control
 - b) Voltage harmonics produced by synchronous machine
 - c) STATCOM (6,6,6)