

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

B.E. Sem-III Remedial Examination March 2010

Subject code: 131101

Subject Name: Basic Electronics

Date: 09 / 03 / 2010

Time: 3.00 pm – 05.30 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

Q.1 (A) What is transition capacitance of a p- n junction diode ? For a step graded junction prove that the expression for the transition capacitance of a diode is same as the capacitance of a parallel plate capacitor. **07**

(B) How does the designer minimize the percentage variation in I_C , due to variation in I_{CO} and V_{BE} and due to variation in β in transistor amplifier circuit. **07**

Q.2 (A) A 230 V , 50 Hz AC voltage is applied to the primary of a 5:1 step down transformer which is used in a bridge rectifier having a load resistor of a value 470 Ω . Assuming the diodes to be ideal , determine the following **07**

- (a) DC output voltage
- (b) DC power deliver to the load
- (c) Maximum value of output current
- (d) Average value of output current
- (e) RMS value of output current
- (f) Output frequency
- (g) PIV of diode

(B) Define **07**

- (a) Drift velocity of electron
- (b) Electric field
- (c) Photovoltaic potential
- (d) Photo excitation
- (e) Photo ionization
- (f) Intensity of electric field
- (g) Reverse recovery time of diode

OR

(B) Define **07**

- (a) Electron volt
- (b) Potential
- (c) Critical wavelength for semiconductor
- (d) Mean life time of carrier
- (e) Mobility of electron
- (f) Volt equivalent of temperature
- (g) Pinch off voltage of FET

- Q.3 (A)** A bar of silicon 0.2 cm long has a cross sectional area of $9 \times 10^{-8} \text{ m}^2$, heavily doped with phosphorus. What will be the majority carrier density resulting from doping if the bar is to have resistance of 2 k Ω ? Given for silicon at room temperature :

$$\mu_n = 0.14 \text{ m}^2/\text{V-sec}, \mu_p = 0.05 \text{ m}^2/\text{V-sec}, n_i = 1.5 \times 10^{10} / \text{cm}^3, q = 1.602 \times 10^{-19} \text{ C}$$

- (B)** Give minimum four comparisons of following semiconductor devices **06**
- (1) Tunnel diode with conventional diode.
 - (2) LED with conventional diode.
 - (3) LED with photo diode.
- (C)** Prove that current density is proportional to product of charge density , mobility of charge and electric field intensity. **04**


OR

- Q.3 (A)** A static resistance of 4 Ω is observed in an ideal germanium diode at room temperature. The current flowing through the diode is 50mA. If the forward biased voltage is 0.2V , volt equivalent temperature is 26mV , calculate :


- (i) Reverse saturation current
- (ii) Dynamic resistance of diode

- (B)** Draw output waveform of following circuits. Consider input of 20V (peak to peak), 10kHz sine wave and assume ideal diode. **06**

(i)

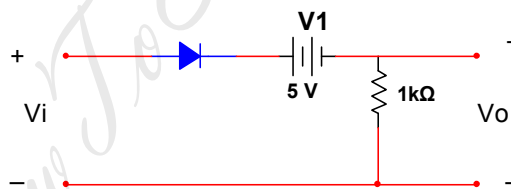


(ii)

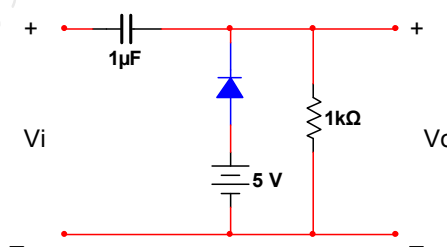

- (C)** Explain the hall effect in semiconductor. How hall effect is considered in measurement of mobility and conductivity? **04**


- Q.4 (A)** Derive relationship between α_{dc} and β_{dc} of a transistor. **04**
- (B)** Explain any one circuit which is used to improve the input impedance of the amplifier. **06**

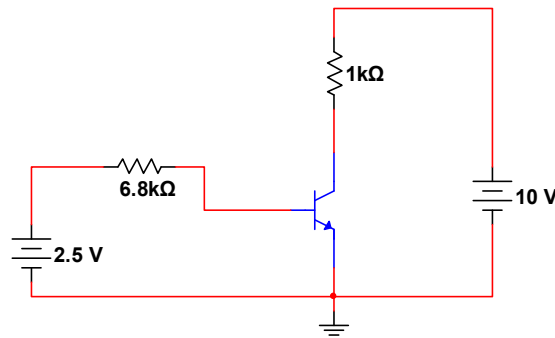- (C) Determine whether or not the transistor in below circuit is in saturation. Assume $\beta = 50$ and $V_{CE(sat)} = 0.3V$, $V_{BE} = 0.7V$. **04**




OR

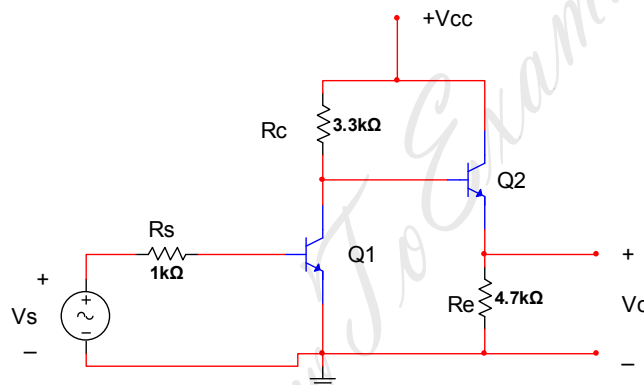- Q.4 (A)** Compare various transistor amplifier configurations. **04**
- (B)** Draw and explain the input and output characteristics of p-n-p silicon transistor in CB configuration. Indicate cut off, saturation and active regions. **06**
- (C)** Two stage amplifier circuit is mentioned below. Calculate overall voltage gain A_v . Take $h_{ie} = 2.2K$, $h_{fe} = 60$, $h_{re} = 2.5 \times 10^{-4}$, $h_{oe} = 2.5 \mu A/V$, $R_c = 3.3 k\Omega$, $R_e = 4.7k\Omega$, $R_s = 1 k\Omega$, $V_{cc} = +12V$. **04**



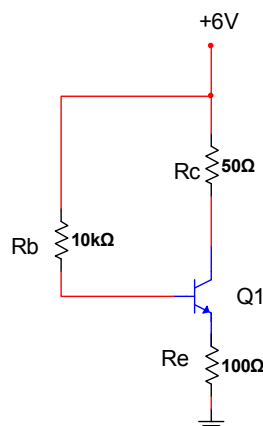- Q.5 (A)** For following circuit, calculate the minimum and maximum value of emitter current when β of transistor varies from 75 to 150. Also calculate the corresponding values of collector to emitter voltage. Take $V_{BE} = 0.3V$, $R_b = 10k\Omega$, $R_c = 50 \Omega$, $R_e = 100 \Omega$, $V_{cc} = +6V$. **06**



- (B)** Explain with neat circuit diagram, the working of a transformer coupled class A power amplifier. **04**

- (C) Compare FET with BJT in terms of advantages, disadvantages, construction and operation. 04

OR

- Q.5 (A) Describe briefly the construction and working of p channel enhancement MOSFET. Draw its characteristic and transfer curve. 06

- (B) A class B push pull amplifier supplies power to a resistive load of 15Ω . The output transformer has a turns ratio of 5:1 and efficiency of 78 %. Assume $h_{fe} = 25$ and $V_{cc} = 18V$. 06

Obtain :

- (a) Maximum power output
- (b) Maximum power dissipation in each transistor
- (c) Maximum base current for each transistor.

- (C) Explain the signification of following parameters in evaluating the regulation performance of a DC series regulator 02

- (a) Input regulation factor (Stability factor) S_V
- (b) Temperature stability factor (Temperature coefficient) S_T
